

## Chapter 6 - BJTs

Threshold voltage:  $V_T \approx 25.9 \text{ mV}$ .

Two junctions in BJT, EBJ (Emitter Base Junction) and CBJ (Collector Base Junction).

Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

### NPN TRANSISTOR:

In the cutoff mode:

$$V_{BC} < 0.4 \text{ V} \mid V_{BE} < 0.5 \text{ V} \mid$$

$$I_C = 0 \mid I_B = 0$$

In the active mode:

$$V_{BC} < 0.4 \text{ V} \mid V_{BE} \approx 0.7 \text{ V} \mid V_{CE} > 0.3 \text{ V}$$

$$I_C = \beta I_B \mid I_B > 0$$

In the saturation mode:

$$V_{BC} \approx 0.5 \text{ V} \mid V_{BE} \approx 0.7 \text{ V} \mid$$

$$V_{CE_{SAT}} \approx 0.2 \text{ V}$$

$$I_C = \beta_{forced} I_B \mid I_B > 0$$

### PNP TRANSISTOR:

In the cutoff mode:

$$V_{CB} < 0.4 \text{ V} \mid V_{EB} < 0.5 \text{ V} \mid$$

$$I_C = 0 \mid I_B = 0$$

In the active mode:

$$V_{CB} < 0.4 \text{ V} \mid V_{EB} \approx 0.7 \text{ V} \mid V_{EC} > 0.3 \text{ V}$$

$$I_C = \beta I_B \mid I_B > 0$$

In the saturation mode:

$$V_{CB} \approx 0.5 \text{ V} \mid V_{EB} \approx 0.7 \text{ V} \mid$$

$$V_{EC_{SAT}} \approx 0.2 \text{ V}$$

$$I_C = \beta_{forced} I_B \mid I_B > 0$$

Current relationships in a BJT transistor.

$I_S$  is known as Saturation Current

$$i_E = i_C + i_B \mid i_E = \frac{\beta+1}{\beta} i_C \mid i_C = \alpha i_E \mid$$

$$\alpha = \frac{\beta}{\beta+1} \mid \beta = \frac{\alpha}{1-\alpha}$$

$\alpha$  is the **common-base current gain**.

A BJT is in the Saturation Region if - The

CBJ is Forward biased by more than 0.4V

- The Ratio of  $i_C/i_B$  is lower than  $\beta$

$$i_C = I_S e^{v_{BE}/V_T}$$

Considering the Early voltage

$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$r_o = \left[ \frac{\delta i_C}{\delta v_{CE}} \Big|_{V_{BE}=\text{constant}} \right]^{-1}$$

$$r_o = \frac{V_A + V_{CE}}{I_C}$$

$$r_o = \frac{V_A}{I'_C}$$

Where  $I'_C = I_S e^{V_{BE}/V_T}$

$$R_{CE_{SAT}} \equiv \frac{\delta v_{CE}}{\delta i_C} \Big|_{i_B=I_B \mid i_C=I_{C_{SAT}}}$$

Amplifier stuff

$$v_{CE} = V_{CC} - i_C R_C$$

Operating point Q occurs at  $(V_{BE}, V_{CE})$ .

$$A_v = - \left( \frac{I_C}{V_T} \right) R_C = - \frac{V_{RC}}{V_T}$$

$$V_{RC} = V_{CC} - V_{CE}$$

$$A_{vmax} \approx \frac{V_{CC}}{V_T}$$

Small signal stuff

$$i_C = I_C + \frac{I_C}{V_T} v_{be}$$

$$i_C = I_C + i_c$$

$$i_c = \frac{I_C}{V_T} v_{be}$$

$$i_c = g_m v_{be}$$

$$g_m = \frac{I_C}{V_T}$$

Base current:

$$i_B = \frac{i_C}{\beta} = \frac{I_C}{\beta} + \frac{1}{\beta} \frac{I_C}{V_T} v_{be}$$

$$i_B = I_B + i_b$$

$$i_b = \frac{1}{\beta} \frac{I_C}{V_T} v_{be}$$

We know that  $I_C/V_T = g_m$  so

$$i_b = \frac{g_m}{\beta} v_{be}$$

The small-signal input resistance looking into the base, is denoted by  $r_\pi$  and is defined as

$$r_\pi \equiv \frac{v_{be}}{i_b} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

Emitter current:

$$i_E = \frac{i_C}{\alpha} = \frac{I_C}{\alpha} + \frac{i_c}{\alpha}$$

$$i_E = I_E + i_e$$

$$i_e = \frac{i_c}{\alpha} = \frac{I_C}{\alpha V_T} v_{be} = \frac{I_E}{V_T} v_{be}$$

Small-signal resistance looking into the emitter is

$$r_e \equiv \frac{v_{be}}{i_e}$$

$$r_e = \frac{V_T}{I_E}$$

$$r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

Relationship between  $r_\pi$  and  $r_e$ :

$$v_{be} = i_b r_\pi = i_e r_e$$

$$r_\pi = (i_e/i_b) r_e$$

$$r_\pi = (\beta + 1) r_e$$

Voltage gain of the amplifier:

$$A_v \equiv \frac{v_{ce}}{v_{be}} = -g_m R_C$$

$$A_v = -\frac{I_C R_C}{V_T}$$

Hybrid- $\pi$  model includes the  $r_\pi$  resistor:

$$i_e = \frac{v_{be}}{r_\pi} + g_m v_{be}$$

$$\frac{v_{be}}{r_\pi} (1 + g_m r_\pi)$$

$$g_m v_{be} = g_m (i_b r_\pi)$$

T-model includes the  $r_e$  resistor:

$$g_m = I_C/V_T$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m}$$

If we include  $r_o$ , the output voltage becomes:

$$v_o = -g_m v_{be} (R_C \parallel r_o)$$

Three different amplifier configurations:

**Common-emitter**

**Common-base**

**Common-collector** (also known as emitter follower)

But first, for all amplifier configurations:

$$R_{in} \equiv \frac{v_i}{i_i}$$

$$v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$$

$$A_{vo} \equiv \frac{v_o}{v_i} \Big|_{R_L=\infty}$$

$$R_x = \frac{v_x}{i_x}$$