

1a)

Write a combination truth and function table for the devices in Figure 5-1 assuming inputs and outputs are active low.

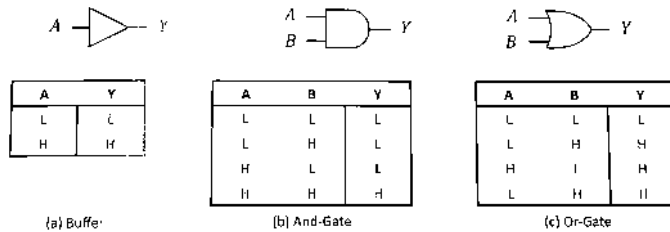


Figure 5-1 Symbols and Function Tables for the Three Basic Logic Devices.

OR

A	B	A.L B.L	(A+B).L	A+B
L	L	H	H	L
L	H	H	L	H
H	L	L	L	H
H	H	L	L	H

Buffer

A	A.L	Y.L	Y
L	H	H	L
H	L	L	H

And

A	B	A.L B.L	AB.L	AB
L	L	H	H	L
L	H	H	H	L
H	L	L	H	L
H	H	L	L	H

2a)

Consider the devices below and write a function table for each of them.

## CHAPTER 5



A	$\bar{A}$
L	H
H	L

A	B	$\bar{A}$	$\bar{B}$	$\bar{A}\bar{B}$	$\overline{\bar{A}\bar{B}}$
L	L	H	H	H	L
L	H	H	L	L	H
H	L	L	H	L	H
H	H	L	L	L	H

A	B	$\bar{A}$	$\bar{B}$	$\bar{A}+\bar{B}$	$\overline{\bar{A}+\bar{B}}$
L	L	H	H	H	L
L	H	H	L	H	L
H	L	L	H	H	L
H	H	L	L	L	H

b)

For each device, tell whether the function table defines a new device or one that has already been presented in this chapter.

Buffer

OR Gate

AND Gate

3)


Complete table 5-1

Table 5-1 Combination Truth and Function Table for Figure 5-7.

A	B	C	A.L	B.H	C.H	A.H	B.L	$\bar{A}.H$	$\bar{A}\bar{B}.H$	F.L	F
0	0	0	H	L	L	L	H	L	L	H	0
0	0	1	H	L	H	L	H	L	L	H	0
0	1	0	H	H	L	L	L	H	L	L	1
0	1	1	H	H	H	L	L	H	L	L	1
1	0	0	L	L	L	H	H	L	L	H	1
1	0	1	L	L	H	H	H	L	L	H	1
1	1	0	L	H	L	H	L	L	H	L	0
1	1	1	L	H	H	H	L	L	L	H	1

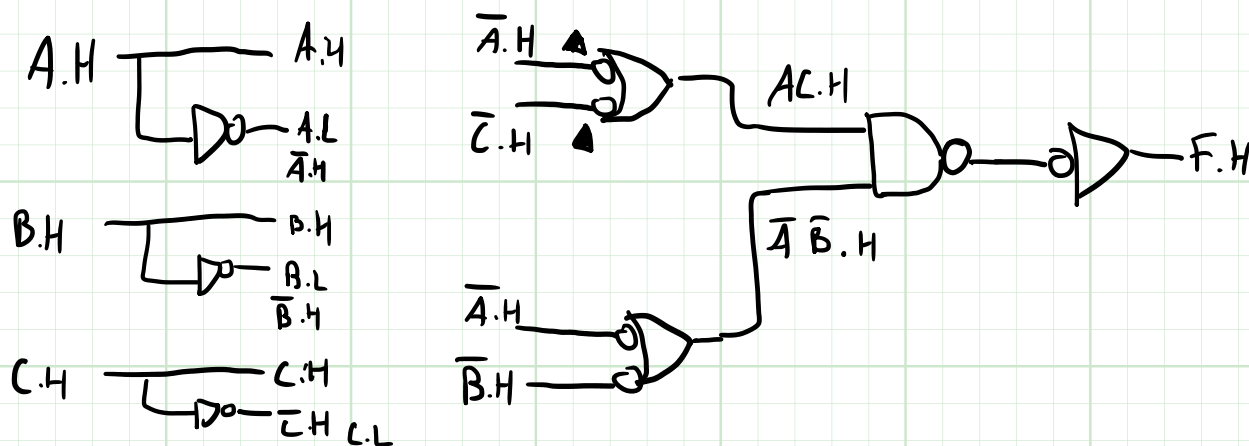4)


Design a logic circuit for  $F = AC + \bar{A}\bar{B}$  assuming A, B, C and F are active high. Use only NAND and NOR and/or inverters.



- 8) Design a logic circuit for the logic equation in Eq 3.25 using only nand- or nor-gates. Assume all inputs are active high and the output, PRIME, is active low.

Eq. 4.25

$$PRIME = \overline{B_2} B_1 + B_2 B_0$$

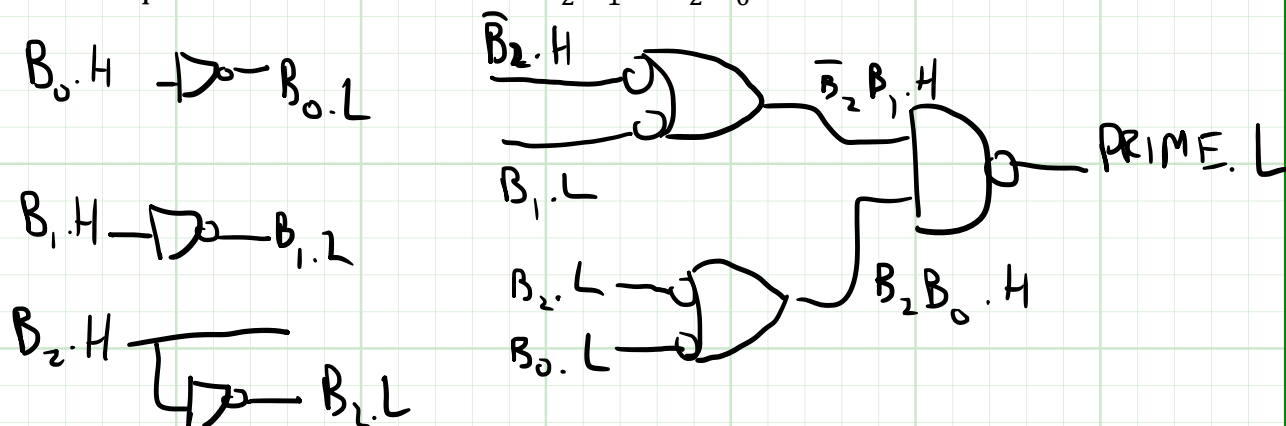

- 10) Show how to implement a 3-input NAND gate using MOSFETs.

