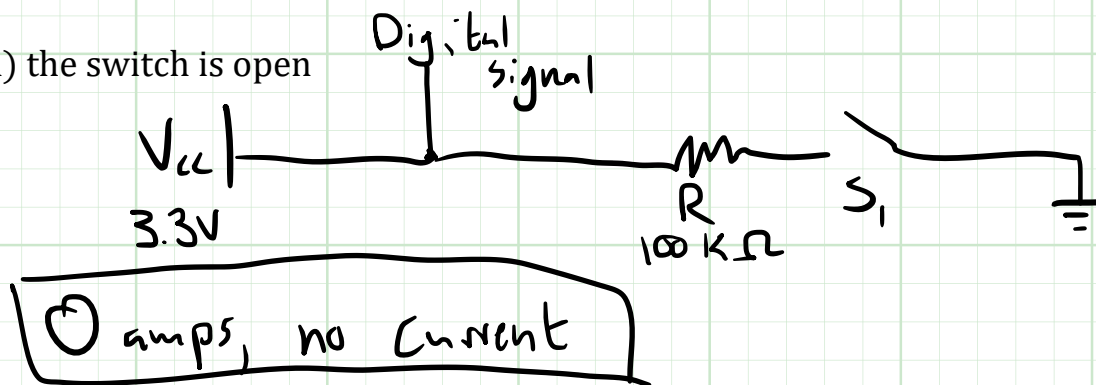



1a)

A $100\text{k}\Omega$ resistor is used in conjunction with a switch to produce a digital signal. If V_{CC} is 3.3V , how much current that flows through the resistor when

(a) the switch is open



b) The switch is closed

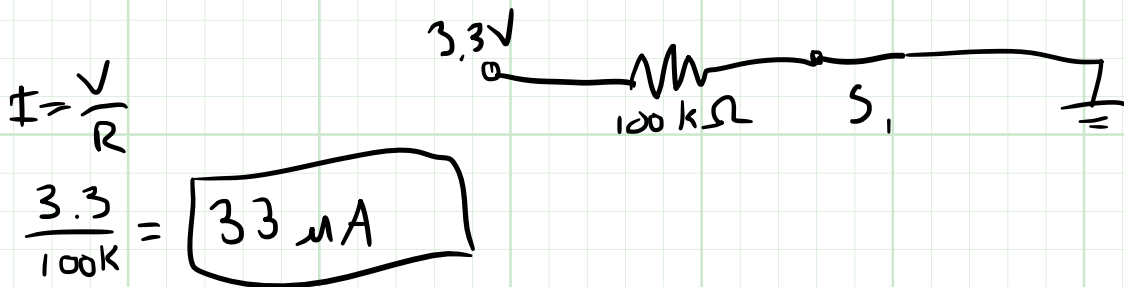

2)


A switch is used to drive a digital signal, but the maximum current through the switch is limited to $1\ \mu\text{A}$. Assuming V_{CC} is 3.3V , what is the minimum size of resistor that should be used?

$$V = IR \quad 3.3 = 1\text{E-}6 \cdot R \quad R = \frac{3.3}{1\text{E-}6}$$

Handwritten answer: $R = 3.3\ \text{M}\Omega$

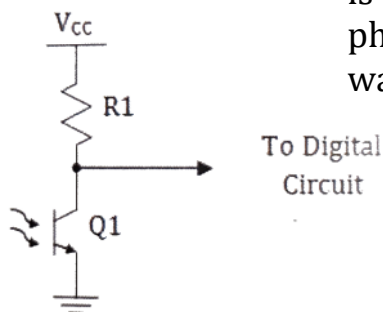
3)

If a phototransistor is connected as in Figure 3-5, what is the voltage level (high or low) if light is striking the phototransistor? (Assume the light is the correct wavelength.)





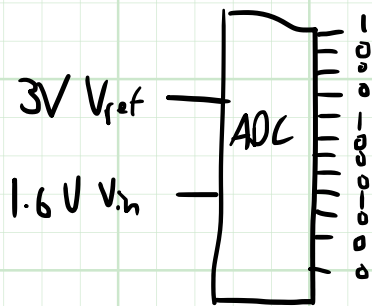- 4b) A load cell is a device that generates a voltage proportional to the force that is applied to it. Suppose the load cell produces a 2V output when the force is 10,000N. If the load cell is connected to a 12-bit ADC with a voltage reference of 3V, what is the ADC output when the force is 8000N? From part A, the voltage is 1.6V at 8000N.



$$D = \left\lfloor \left(\frac{V_{in}}{V_{ref}} \right) 2^N \right\rfloor$$


$$= \left\lfloor \frac{1.6}{3} \cdot 2^{12} \right\rfloor = 2184$$

$$= 0b100010001000$$

- 5) An oxygen sensor generates an analog voltage of 13mV per percent O_2 (i.e. the voltage would be 1.3V in a pure oxygen environment). At what voltage should the negative input of a comparator be set so that its digital output goes low when the percentage of oxygen drops below 15%?

$$15 \cdot 13mV = 195mV$$

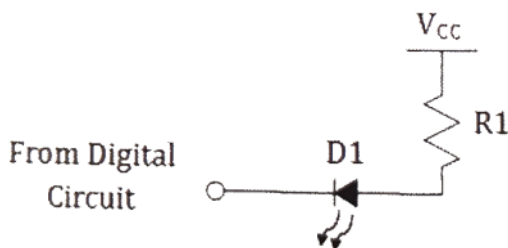- 6) An LED is driven from a digital signal as shown in Figure 3-8. If $V_f = 1.8V$, $I = 10mA$, and $V_{CC} = 5.0V$, what resistor value should be used? Assume the digital signal is 0.3V when it is low.



$$\frac{V_{CC} - V_f - 0.3}{R_1} = I$$

$$\frac{5.0 - 1.8 - 0.3}{R_1} = 10mA$$

$$\frac{2.9}{10mA} = R_1$$

$$R_1 = 290\Omega$$

$$(R_1 = 240 \Omega)$$

9) Go online. Find and list a manufacturer and part number for each of the following devices:

b) An opto-isolator

Toshiba TLP2745

c) A comparator

STMicroelectronics LM393DT

